

+ follow



# **\$3 Diode clip Distortion-DIY Eurorack Modular Synthesizer**

 $\bigcirc$  7










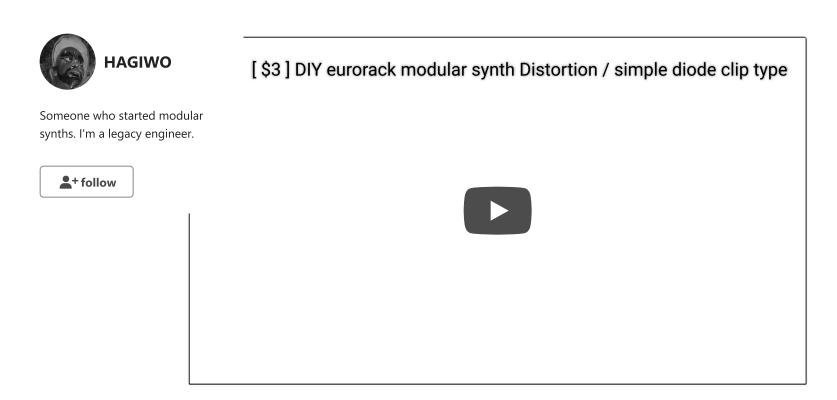I made my own diode clip distortion for the modular synthesizer, so it's a memoir.



## background

The 45th work of his own modular synth.

So far, I've made a few DSP effect modules myself, but not an analog one yet. In the future, I would like to challenge the analog effect module. First of all, I decided to create a simple distortion module.

The combination of synthesizers and distortions is often used in techno music.

on from Prophet 5, like the one I used in YMO's "music plan."



Someone who started modular synths. I'm a legacy engineer.



音楽の計画 (2019 Bob

YELLOW MAGIC ORCHESTRA

**PREVIEW** 



## :s of the production



ck Standard 3U 6HP Size

Power Supply: Requires dual 12V power supply  $\pm$  25mA or less (at +12V) / 25mA or less (at -12V).

The current consumption has not been accurately measured, but an approximate value is estimated from the current consumption indicated by the regulated power supply.







#### Attenuates **ATTN**

input audio. The audio signal of modular synths is generally 5 V  $\pm$ . On the other hand, in the distortion of the diode clip, the effect begins when the audio signal exceeds  $\pm 0.6$  V.

Therefore, the audio signal must be attenuated to less than  $0.6V \pm before$  reaching the diode clip circuit.

Since it is possible to attenuate even with the variable resistance of the amplifier amplifier circuit, it is not always necessary to prepare an attenuator.

My homebrew module has a wide voltage range, from a  $\pm 1V$  audio signal to a  $\pm 5V$  signal, so I added an ATTN function.



Someone who started modular synths. I'm a legacy engineer.



on. Because it is a simple clip circuit using a diode, when distortion is I, the waveform pile is collapsed, and the overtone increases.




Is the amplification rate of **GAIN** 

output audio. By passing through the diode clip circuit, the audio signal is attenuated to less than  $\pm 0.6$  V. By amplifying with GAIN, it amplifies to the audio voltage level of the modular synth.



+ follow

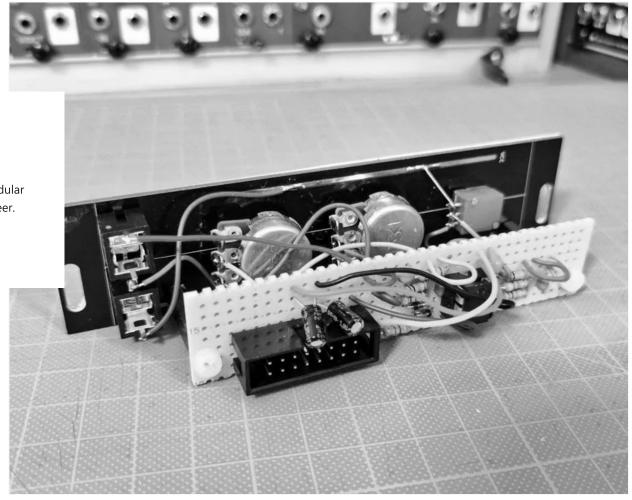

## **Production cost**

Total amount about 330 yen-----

front panel 100 yen variable resistance, 110 yen op amp 30 yen

#### are the link below



Someone who started modular synths. I'm a legacy engineer.

+ follow

#### ュラーシンセ自作で使う安価な部品一覧


ついでに。適時更新。コストと品質の観点で記載、主観による。alie はリンクを貼ってもすぐに切れるので、画像で残す。値段は購入当 の。昨今は値動きが激しい。品質は私の経験値。よって母数は数…





A very simple configuration consisting of an op amp, resistor, capacitor, and diode.

### hardware

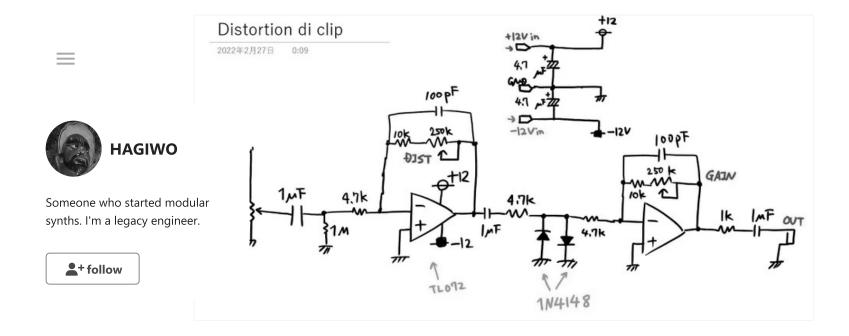


Attenuated (ATTN), amplified (DIST), attenuated (diode clip), amplified (GAIN), and so on.

I just reviewed the distortion effectors used in electric guitars and the constants for modular synths. The modular synth can use -12V and does not require a voltage offset circuit like a guitar effector, so the circuit configuration is simpler than a guitar effector.

The 100pF capacitor in the op amp circuit is a countermeasure against oscillation. Without it, it will oscillate.

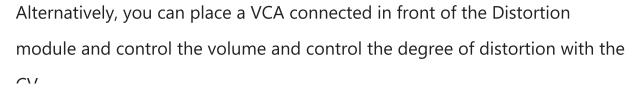If you want to control the distortion with a CV, you can replace the DIST circuit with a VCA like the LM13700.







## licity: Please support open source projects

r to continue the open source project of DIY modular synths, we are ng patrons with a service called patreon.

I would be happy if you could help me with a cup of coffee.

We also distribute patron-only content.

## **HAGIWO** is creating DIY eurorack modular synth esizer | Patreon

Become a patron of HAGIWO today: Get access to exclusive cont www.patreon.com